



VIT

Vellore Institute of Technology

(Deemed to be University under section 3 of UGC Act, 1956)

CHENNAI

246261858

Final Assessment Test(FAT) - Apr/May 2025

Programme	B.Tech.	Semester	Winter Semester 2024-25
Course Code	BECE203L	Faculty Name	Prof. Sivasubramanian A
Course Title	Circuit Theory	Slot	D1+TD1+TDD1
		Class Nbr	CH2024250502882
Time	3 hours	Max. Marks	100

Instructions To Candidates

- Write only your registration number in the designated box on the question paper. Writing anything elsewhere on the question paper will be considered a violation.

Course Outcomes

CO1: Apply the knowledge of various circuit analysis techniques such as mesh analysis, nodal analysis, and network theorems to investigate the given network.

CO2: Analyse the resonance and transient response of the first order, second order circuits

CO3: Able to solve the networks using graphical approach.

CO4: Design and analyse two-port networks, passive filters and attenuators.

CO5: Able to analyse the given network by transforming from time domain to S domain.

CO6: Analyse the given network using Fourier series and transforming from time domain to frequency domain.

Section - I

Answer all Questions (6 × 15 Marks)

01. (a) Determine the value of I_o in the circuit of Fig.1 using nodal analysis. [8 Marks]

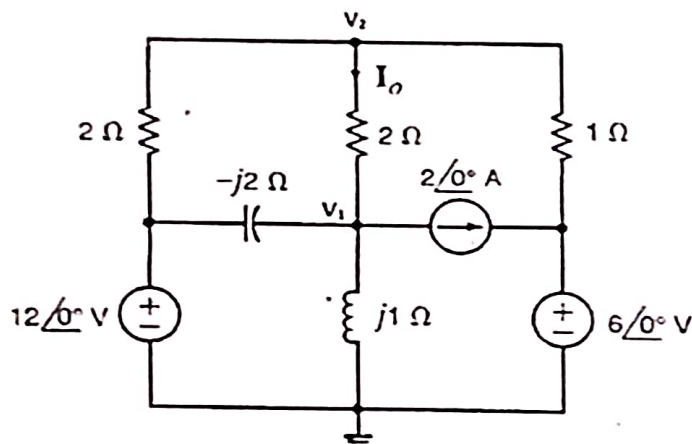


Fig.1

- (b) Use superposition theorem and find V_o in the network of Fig.2. [7 Marks]

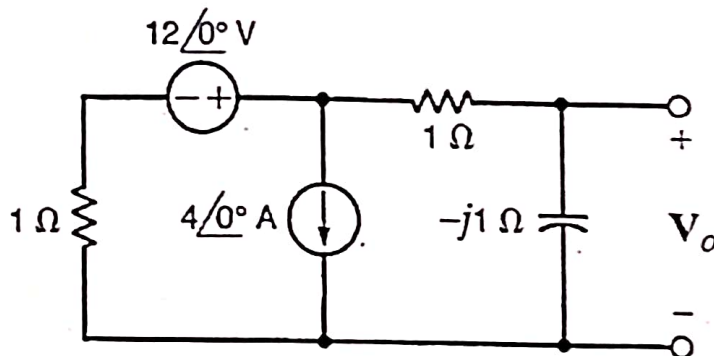


Fig.2

02. (a) Consider the switch in the circuit of Fig.3 has been in position 1 for a long time, and at time $t = 0$ the switch is moved to position 2. Determine the voltage across the capacitor for $t > 0$. [6 Marks]

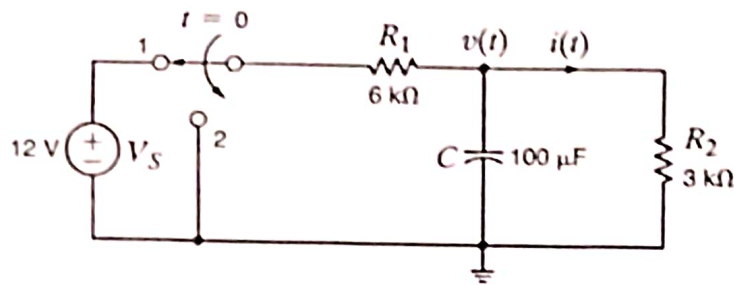


Fig.3

- (b) Consider a parallel RLC circuit with $R = 2 \Omega$, $L = 1 \text{ H}$, and $C = 10 \text{ mF}$. Find the voltage response $v(t)$, across the capacitor, for $t > 0$ if the initial voltage of capacitor at time $t = 0$ is $V_0 = 50 \text{ V}$ and the initial current of the inductor at time $t = 0$ is $I_0 = 0 \text{ A}$. [9 Marks]

[15] (CO2/K4)

03. Find the h-parameters of the circuit shown in Fig. 4. Draw an equivalent circuit of the same. [15 Marks]

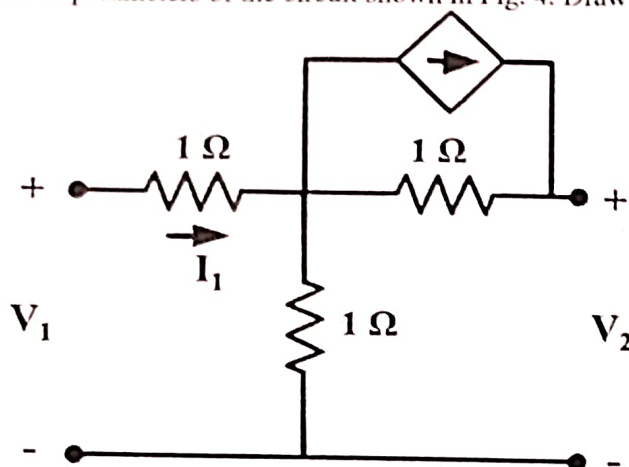


Fig.4

[15] (CO4/K3)

04. (a) Show that a series RL circuit is a low pass filter if the output is taken across the resistor. Calculate the corner frequency f_c if $L = 2 \text{ mH}$ and $R = 10 \text{ k}\Omega$. [5 Marks]

- (b) Design an RL high pass filter that uses a 40-mH coil and has a cutoff frequency of 5 kHz. [5 Marks]

- (c) Design a symmetrical lattice attenuator to have an attenuation of 20 dB, to work with a line having characteristic impedance of 800Ω . [5 Marks]

[15] (CO4/K2)

05. (a) Solve the circuit in Fig.5 using Laplace transform and find current i_L . [9 Marks]

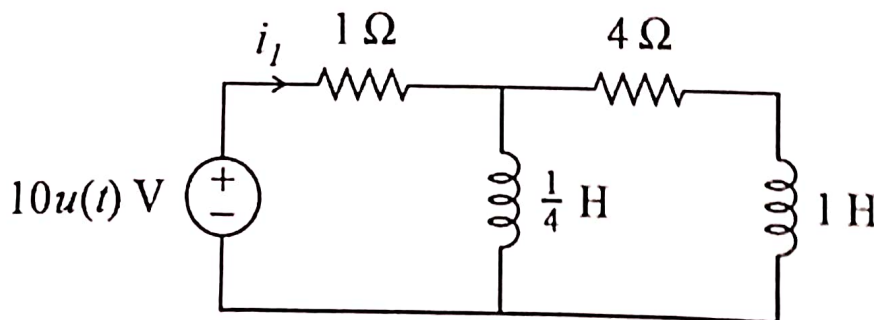


Fig.5

- (b) When the input to a system is a unit step function, the response is $10 \cos 4t u(t)$. Obtain the transfer function of the system. [6 Marks]

[15] (CO5/K3)

06. (a) Find the Fourier Series representation of the input signal $v_{in}(t)$ shown in Fig.6. [8 Marks]

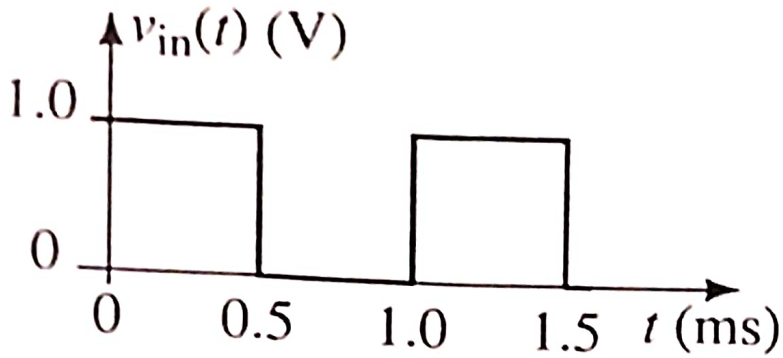


Fig.6

- (b) Using the obtained Fourier Series in (a), determine the output voltage v_{out} of the circuit shown in Fig.7. [7 Marks]

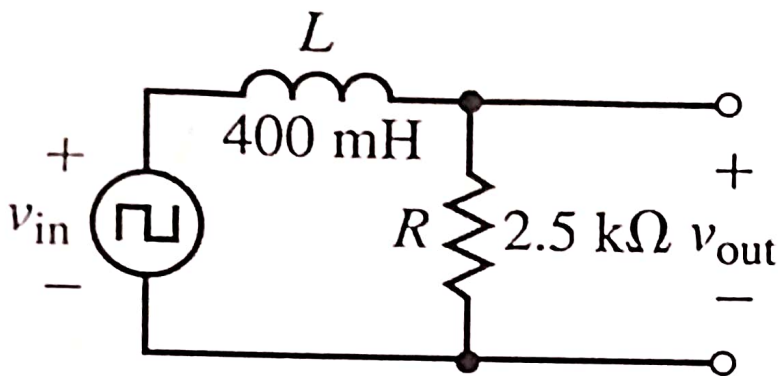


Fig.7

$$\begin{matrix} a. \\ b. \\ c. \\ d. \end{matrix} \begin{bmatrix} 1 & 2 & 3 & 4 & 5 & 6 & 7 & 8 & 9 & 10 \\ -1 & 1 & 0 & & & & & & & \end{bmatrix}$$

[15] (CO6/K3)

Section - II

Answer all Questions (1 × 10 Marks)

07. For the network graph given in Fig.8, write the tie-set and cut-set matrix. Take the twigs of the tree as branches 1, 2, 7, 8. [10 Marks]

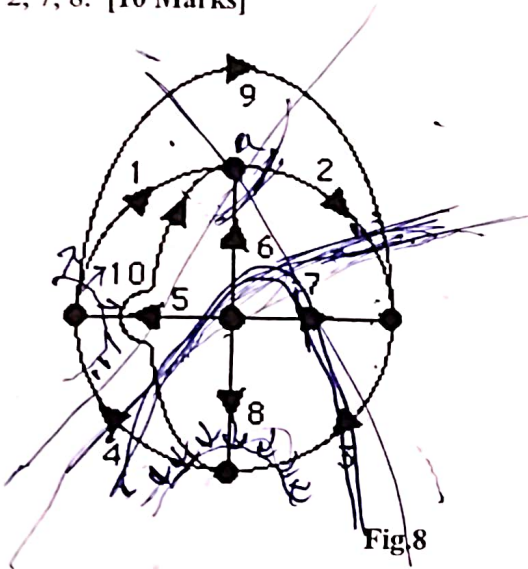


Fig.8

$$\begin{matrix} 1 \\ 2 \\ 7 \\ 8 \end{matrix} \begin{bmatrix} 1 & 2 & 3 & 4 & 5 & 6 & 7 & 8 & 9 & 10 \\ 1 & 0 & 0 & -1 & -1 & 0 & 0 & 0 & 0 & 0 \\ 0 & 1 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 1 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 1 & 0 & 0 & 0 & 0 & 0 & 0 \end{bmatrix}$$

[10] (CO3/K3)

BL-Bloom's Taxonomy Levels - (K1-Remembering, K2-Understanding, K3-Applying, K4-Analysing, K5-Evaluating, K6-Creating)

