



VIT[®]

Vellore Institute of Technology
(Deemed to be University under section 3 of UGC Act, 1956)

Continuous Assessment Test – 1, August 2024

Programme	: B. Tech. CSE	Semester	: Fall 2024 - '25
Course	: Basic Electrical and Electronics Engineering	Code	: BEEE102L
Faculty	: D. R. Binu Ben Jose	Slot	: C1+TC1
	Common question across C1 slot		Class Number : CH2024250103732
Time	: 1 $\frac{1}{2}$ Hours	Max. Marks	: 50

Answer ALL the Questions (5 x 10 = 50 Marks)

1. Use mesh analysis to find V_o marked in the circuit shown in Fig. 1. (10)

 


Fig. 1

2. Find the voltages v_1 and v_2 marked in the circuit shown in Fig. 2 using nodal analysis. (10)

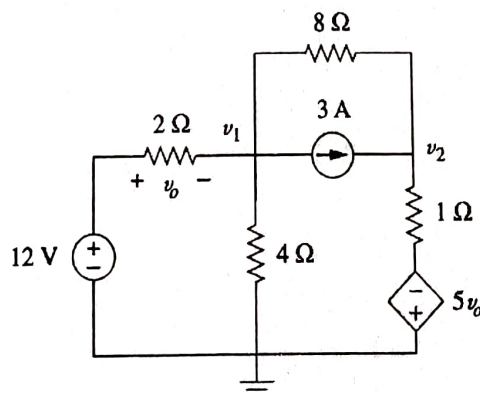


Fig. 2

3. Compute the **current** i marked in the circuit shown in Fig. 3 using (10) Superposition principle.

 


Fig. 3

4. In the circuit in Fig. 4, a load resistance of value $10\ \Omega$ is connected across the terminals **a-b**.

(a) For what value of load resistance will the maximum power be delivered to the load? (4)

(b) Compute the maximum power that can be delivered by the circuit. (6)

 


Fig. 4

5. A load impedance Z is connected across a voltage source

$$v(t) = 12 \sin(10t + 20^\circ) \text{ V}.$$

(a) If the current drawn by the load is $i(t) = 5 \cos(10t - 30^\circ) \text{ A}$, find the phase angle between voltage and current. Comment on whether the current leads or lags the voltage. (4)

(b) If the load consists of a resistor $R = 5\ \Omega$, an inductor $L = 0.2 \text{ H}$ and a capacitor $C = 0.1 \text{ F}$ are connected in series, compute the current drawn by the load. (6)

↔↔↔